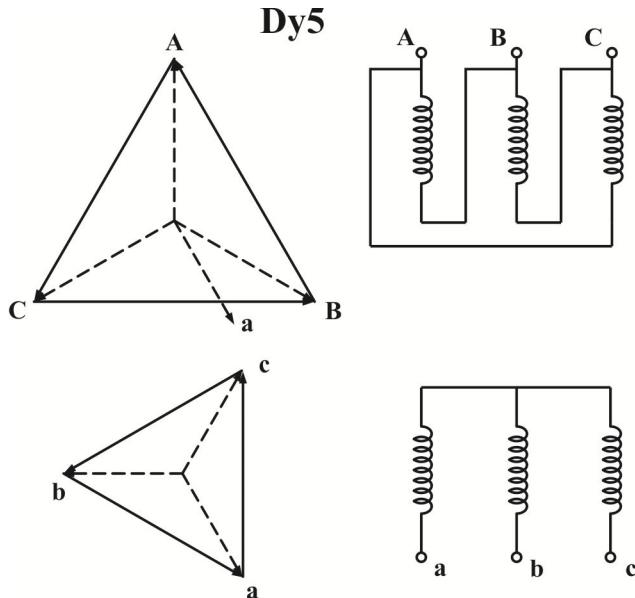


ЕНЕРГЕТСКИ ТРАНСФОРМАТОРИ (ОГЗЕТ)
- колоквијум-децембар 2014 -

Београд, 21.11.2014.

- РЕШЕЊА -

1. a)



$$6) N_2 = N_1 \frac{U_{02}}{\sqrt{3}U_{1n}} = 2480 \frac{400}{\sqrt{3} \cdot 35 \cdot 10^3} \approx 17$$

$$B_m = \frac{U_{1n}}{4,44 f N_1 k_{Fe} S_{Fe}} = \frac{35000}{4,44 \cdot 50 \cdot 2480 \cdot 0,95 \cdot 400 \cdot 10^{-4}} = 1,67 T$$

2. a) теорија

$$6) P_{vn} = \frac{P_{0n}}{3} = \frac{1420}{3} = 473,3 W$$

$$P_v \sim U^2 \Rightarrow P_v' = P_{vn}$$

$$P_h \sim \frac{U^n}{f^{n-1}} \Rightarrow P_h' = P_{hn} \left(\frac{f_n}{f'} \right)^{n-1} = 2 \cdot 473,3 \cdot \left(\frac{50}{60} \right) = 788,8 W$$

$$P_{Fe}' = P_h' + P_v' = 1262 W$$

$$3. I_{2nf} = \frac{S_n}{\sqrt{3} \cdot U_{2n}} = \frac{630 \cdot 10^3}{\sqrt{3} \cdot 400} = 909,3 A$$

$$R_a'' = \frac{U_{0f}^2}{P_0/3} = \frac{U_0^2}{P_0} = \frac{400^2}{1420} = 112,7 \Omega \quad I_a'' = \frac{U_{0f}}{R_a''} = \frac{400}{\sqrt{3} \cdot 112,7} = 2,05 A$$

$$I_\mu'' = \sqrt{I_0^2 - I_a''^2} = \sqrt{16,4^2 - 2,05^2} = 16,27 A \Rightarrow X_\mu'' = \frac{U_{02}}{\sqrt{3} \cdot I_\mu''} = \frac{400}{\sqrt{3} \cdot 16,27} = 14,19 \Omega$$

$$n = \frac{\sqrt{3} \cdot U_{1n}}{U_{02}} = \frac{\sqrt{3} \cdot 35}{0,4} = 151,6$$

$$R_k = \frac{P_k}{3 \cdot I_{kf}^2} = \frac{P_k}{I_k^2} = \frac{6500}{9^2} = 80,25 \Omega \Rightarrow R_k'' = \frac{R_k}{n^2} = \frac{80,25}{151,6^2} = 3,5 m\Omega$$

$$R_1'' \approx R_2 = \frac{R_k}{2} = 1,75 m\Omega$$


$$Z_k'' = \frac{Z_k}{n^2} = \frac{U_{kf}}{I_{kf} n^2} = \frac{\sqrt{3} \cdot 1715}{9 \cdot 151,6^2} \approx 14,4 m\Omega$$

$$X_k'' = \sqrt{Z_k''^2 - R_k''^2} = \sqrt{14,4^2 - 3,5^2} = 13,97 m\Omega \Rightarrow X_{\sigma 1}'' \approx X_{\sigma 2} = \frac{X_k}{2} = 6,98 m\Omega$$

$$u_k = \frac{U_{kf}}{U_{1nf}} \cdot 100 = \frac{1715}{35000} \cdot 100 = 4,9 \%$$

$$u_{kn} = u_k \% \cdot \left(\frac{I_{1n}}{I_k} \right) = 4,9 \cdot \left(\frac{6\sqrt{3}}{9} \right) = 5,66 \%$$
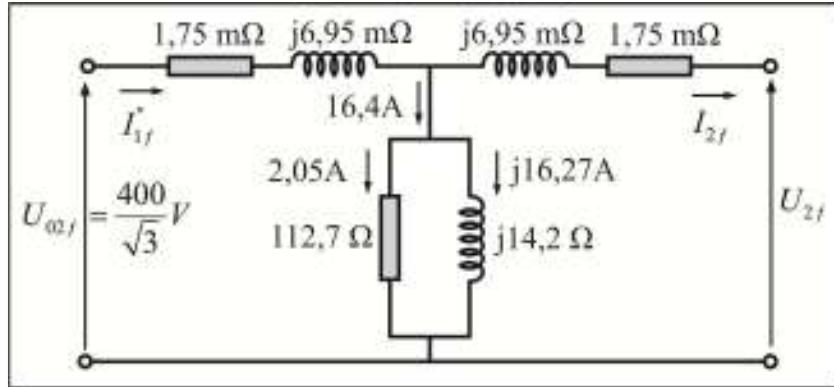
$$P_{kn}^{75} = P_k \left(\frac{I_{1n}}{I_k} \right)^2 = 6500 \cdot \left(\frac{6\sqrt{3}}{9} \right)^2 = 8667 W$$



4. $k_F = 1 + \left(\frac{\pi \mu_0 f}{\rho} \right)^2 \frac{m^2 d^4}{19,4}; \quad \rho_{Cu}^{75^\circ} = \frac{235+75}{235+20} \cdot \frac{10^{-6}}{57} = \frac{10^{-6}}{46,9} \Omega m$

$$k_F^{75^\circ} = 1 + \left(\frac{4 \cdot \pi^2 \cdot 50 \cdot 10^{-7}}{10^{-6}/46,9} \right)^2 \cdot \frac{100 \cdot 1,6^4 \cdot 10^{-12}}{19,4} = 1 + 0,0029 = 1,0029$$

$$P_d^{75^\circ} = \left(1 - \frac{1}{k_F} \right) \cdot P_k^{75^\circ} = 25,1 W$$

$$5. \text{ a) } \beta_m = \sqrt{\frac{P_{0n}}{P_{kn}}} = \sqrt{\frac{1420}{8667}} = 0,4, \cos \varphi = 1$$

$$u_{rn} = \frac{P_{kn}}{S_n} \cdot 100 = \frac{8667}{630 \cdot 10^3} \cdot 100 = 1,38\% \Rightarrow u_x = \sqrt{u_k^2 - u_r^2} = \sqrt{5,66^2 - 1,38^2} = 5,49\%$$

$$\left. \begin{array}{l} a = \beta_m u_{rn} = 0,55\% \\ b = \beta_m u_{xn} = 2,22\% \end{array} \right\} \Rightarrow \Delta u = a + \frac{b^2}{200} = 0,584\%$$

$$U_2 = U_{02} \left(1 - \frac{\Delta u}{100} \right) = 400 \cdot \left(1 - \frac{0,584}{100} \right) = 397,7V$$

$$\eta_{m\%} = \frac{\beta_m \cdot S_n}{\beta_m \cdot S_n + 2P_{0n}} \cdot 100 = \frac{0,4 \cdot 630}{0,4 \cdot 630 + 2 \cdot 1,42} = 98,89\%$$

$$6. \quad \theta_{m1} = \frac{P_{0n} + \beta_1^2 P_{kn}}{P_{0n} + P_{kn}} \cdot \theta_{mn} = \frac{1,42 + 0,8^2 \cdot 8,67}{1,42 + 8,67} \cdot 55 = 38K$$

$$\beta_2 = 0,8 + 0,5 = 1,3 \Rightarrow \theta_{m2} = \frac{P_{0n} + \beta_2^2 P_{kn}}{P_{0n} + P_{kn}} \cdot \theta_{mn} = \frac{1,42 + 1,3^2 \cdot 8,67}{1,42 + 8,67} \cdot 55 = 87,6K$$

$$\theta_2 = \theta_{mn} = \theta_{m2} \left(1 - e^{-t_x/2} \right) + \theta_{m1} e^{-t_x/2} \Rightarrow t_x = 2 \cdot \ln \frac{(\theta_{m2} - \theta_{m1})}{(\theta_{m2} - \theta_{mn})} = 2 \cdot \ln \frac{(87,6 - 38)}{(87,6 - 55)} \approx 50 \text{ min}$$

7. теоријско питање

8. теоријско питање