

10.

ПХ:

$$R''_a = \frac{U_{02f}^2}{P_0/3} = \frac{U_{02}^2}{P_0} = \frac{420^2}{650} = 271,4 \Omega \Rightarrow I''_a = \frac{U_{02f}}{R''_a} = \frac{420}{\sqrt{3} \cdot 271,4} = 0,893 \text{ A}$$


$$I''_0 = j_0 \cdot I_{2nf} = 0,024 \cdot 343,7 = 8,248 \text{ A} \Rightarrow I''_\mu = 8,2 \text{ A} \Rightarrow X''_\mu = \frac{U_{02f}}{I''_\mu} = \frac{420}{\sqrt{3} \cdot 8,2} = 29,6 \Omega$$

КС:

$$R''_k = \frac{P_k}{3I_{2nf}^2} = \frac{3250}{3 \cdot 343,7^2} = 9,2 \text{ m}\Omega \Rightarrow R''_1 = R_2 = \frac{R''_k}{2} = 4,6 \text{ m}\Omega$$

$$Z''_k = \frac{u_k}{100} \frac{U_{02f}}{I_{2nf}} = \frac{4}{100} \cdot \frac{420}{\sqrt{3} \cdot 343,7} = 28,2 \text{ m}\Omega \Rightarrow X''_k = \sqrt{Z''_k{}^2 - R''_k{}^2} = 26,6 \text{ m}\Omega$$
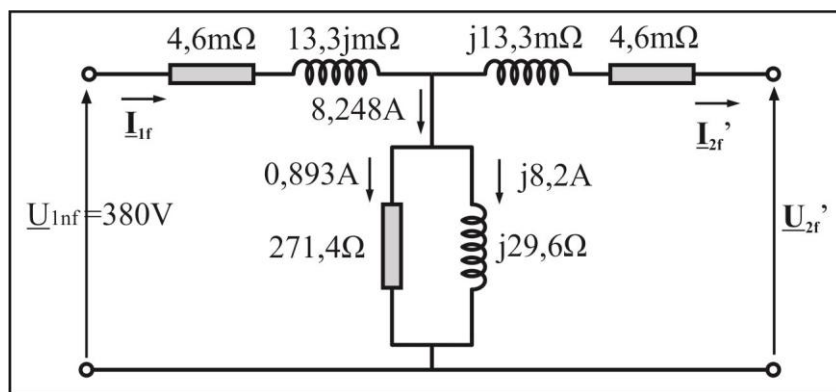
$$\Rightarrow X''_{\sigma 1} = X_{\sigma 2} = \frac{X''_k}{2} = 13,3 \text{ m}\Omega$$



13.

$$u_{rn} = 2,4\%, \quad u_{xn} = 3,81\%$$

a) Индуктивно оптерећење:

$$a = 5,49\%$$

$$b = 1,25\%$$

$$\Delta u = a + \frac{b^2}{200} = 5,5\%$$

$$U_2 = 207,9 \text{ V}$$

б) Капацитивно оптерећење:

$$a = -1,25\%$$

$$b = 5,49\%$$

$$\Delta u = a + \frac{b^2}{200} = -1,1\%$$

$$U_2 = 222,4 \text{ V}$$